

# DRV8800/DRV8801 Design in Guide

#### **ABSTRACT**

This document is provided as a supplement to the DRV8800/DRV8801 datasheet. It details the steps necessary to properly interface the device in most motion control applications powering a DC motor with conventional control signals such as PHASE and ENABLE.

#### Contents 1 1.2 1.3 2 3 3.1 4 4.1 Pulse-Width Modulating PHASE......9 4.2 List of Figures 1 2 3 4 5 6 7



General Description www.ti.com

## 1 General Description

#### 1.1 H-Bridge Motor Driver

The DRV8800/DRV8801 consists of a single H Bridge capable of delivering up to 2.8-A peak current to a single DC motor load in both directions.

The H Bridge is protected against shorts to ground or power input by means of increased current detection.

The device is also protected against increased die temperature by implementing a thermal shutdown mechanism.

The SENSE pin can be used to set the maximum current so that the DC motor will drive at 100% duty cycle. This terminal can be connected to ground for maximum current (peak current limited by Over Current Protection circuitry).

## 1.2 Control Signals

The DRV8800/DRV8801 H Bridge offer PHASE and ENABLE control input lines which allow device users to control direction (with PHASE) and speed (by applying a PWM to the ENABLE pin).

The device also offers an improved means to control current through the motor winding recirculation. MODE 1 and MODE 2 input control signals grant three different degrees of slow/fast decay modes.

## 1.3 Proportional to Current Voltage Output (VPROPI)

The DRV8800/DRV8801 adds an important feature to motion control applications wanting to determine the current level flowing through the DC motor winding. An analog voltage output pin, called VPROPI for voltage proportional to current, supplies a signal which analog to digital converters and microcontroller applications can use to accurately determine how much current is flowing through the controlled DC motor.

#### 2 Thermal Considerations

Although the DRV8800 and DRV8801 are rated at 2.8-A of current handling, the previous only holds true as long as the internal temperature does not exceeds 170°C. In order to operate at this rate, the following measures must be taken under consideration.

# 2.1 Junction-to-Ambient Thermal Impedance ( $\theta_{JA}$ )

The DRV8800RTY/DRV8801RTY device, cased in a QFN package, has a  $\theta_{JA}$  of 42°C/W. At any given time during the steady state portion of the cycle, two FETs are enabled: A high side sourcing FET and a low side sinking FET. Die temperature can then be computed by Equation 1.

$$T_{die} = 42 \frac{{}^{\circ}C}{W} \cdot I_{winding}^{2} \cdot RDS_{ON} \tag{1}$$

The DRV8800PWP/DRV8801PWP device, cased in a HTSSOP package, has a  $\theta_{JA}$  of 33°C/W. At any given time during the steady state portion of the cycle, two FETs are enabled: A high side sourcing FET and a low side sinking FET. Die temperature can then be computed by Equation 2.

$$T_{die} = 33 \frac{{}^{\circ}C}{W} \cdot I_{winding}^{2} \cdot RDS_{ON}$$
(2)



www.ti.com Using VPROPI

## 3 Using VPROPI

The analog output VPROPI offers SENSE current information as an analog voltage proportional to said current. Said feature is only available when a resistor has been placed between the SENSE pin and ground, and a voltage is being drawn across said resistor. The following sections detail the equations required to properly select this resistor and extract the information from the VPROPI output.

## 3.1 Selecting the SENSE Resistor

A SENSE resistor must be connected between the SENSE pin and ground as shown in Figure 1.

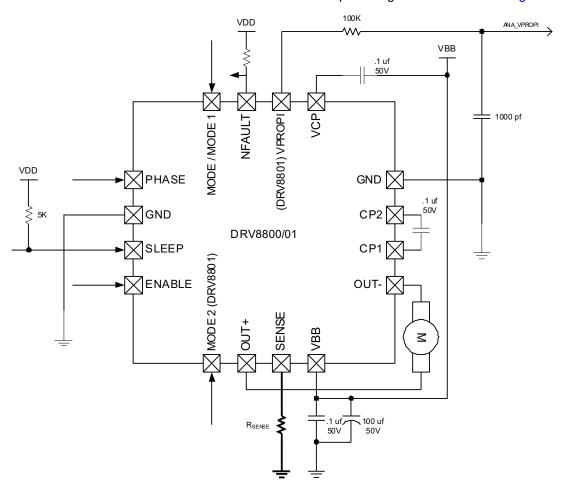


Figure 1. SENSE Resistor Connection

A lack of a resistor (i.e. a direct connection to ground) yields a SENSE voltage equal to zero. In that case, maximum current is 2.8 A and VPROPI outputs 0 V.

A resistor connected as explained before, will yield a VPROPI output as detailed in the next section. The voltage across this resistor has to be smaller than 500 mV. Any voltage equal or larger to 500 mV will signal the device to shut down as trip current has been reached. In this case, device will enter recirculation as stipulated by the MODE input pin (for the DRV8800) or MODE 1 and MODE 2 input pins (for the DRV8801).

Equation 3 shows the value of the resistor to a particular current setting.

$$R_{sense} = \frac{500mV}{I_{trip}} \tag{3}$$



Using VPROPI www.ti.com

# 3.2 VPROPI Output

The analog output VPROPI varies proportionally with the SENSE voltage according to Equation 4.

$$VPROPI = 5 \cdot \left| V_{SENSE} \right| \tag{4}$$

An RC network in series with the VPROPI output is recommended, if this voltage is to be sampled by an analog to digital converter.

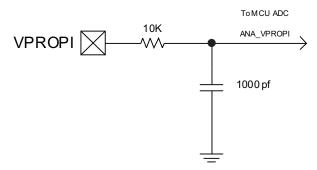


Figure 2. RC Network in Series With the VPROPI Output

It is imperative to realize that VPROPI will decrease to 0 V while the H Bridge enters slow decay recirculation.

www.ti.com Using VPROPI

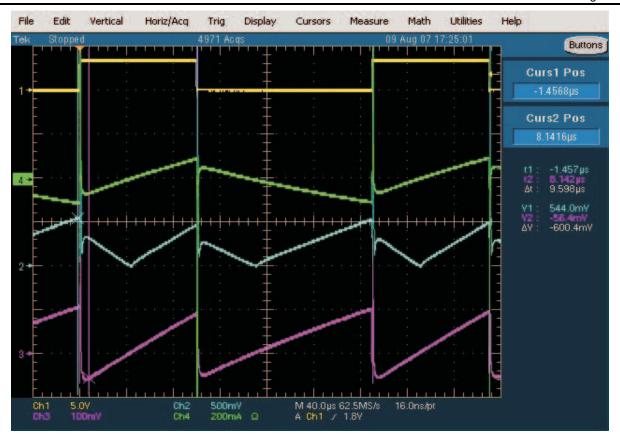


Figure 3. PHASE PWM

Channel 1 is PHASE pin.

Channel 2 is VPROPI analog output.

Channel 3 is SENSE pin.

Channel 4 is winding current.



Using VPROPI www.ti.com



Figure 4. Fast Decay: MODE1 = 0, MODE2 = 0

Channel 1 is PHASE pin.

Channel 2 is VPROPI analog output.

Channel 3 is SENSE pin.

Channel 4 is winding current.

www.ti.com Using VPROPI



Figure 5. Slow Decay: MODE1 = 1, MODE2 = X

Channel 1 is PHASE pin.

Channel 2 is VPROPI analog output.

Channel 3 is SENSE pin.

Channel 4 is winding current.

VPROPI analog output will not offer winding current information while on slow decay mode (MODE1 = 1). In slow decay mode, the lower transistors (MODE2 = 0) or the upper transistors (MODE2 = 1) are enabled. Winding current flow decays through this transistor pair and not through the SENSE resistor. VSENSE = 0 V and VPROPI is 0 V as well.



Micro Processor Interface www.ti.com



Figure 6. VPROPI Limitations During Ground to Source Current Flow

Channel 1 is ENABLE pin.

Channel 2 is SENSE pin.

Channel 3 is VPROPI analog output.

Channel 4 is winding current.

VPROPI analog output is meaningful during current flow with positive polarity (from VBB to SENSE). However, whenever the winding current flows from GND, through the SENSE resistor and into the source (VBB), while it decays, current magnitudes larger than a threshold proportional to the SENSE resistor will trigger parasitic current flow. As a result, winding current is a function of current flowing through the SENSE resistor and current flowing through the parasitic path.

#### 4 Micro Processor Interface

The DRV8800/DRV8801 can be easily controlled with most microcontrollers. At the most, seven I/O pins are required. All of the digital control signals can be handled with conventional GPIO pins configured as outputs. ENABLE and PHASE control signals can be pulse-width modulated by using timers, allowing for proportional direction and speed control.

www.ti.com Micro Processor Interface

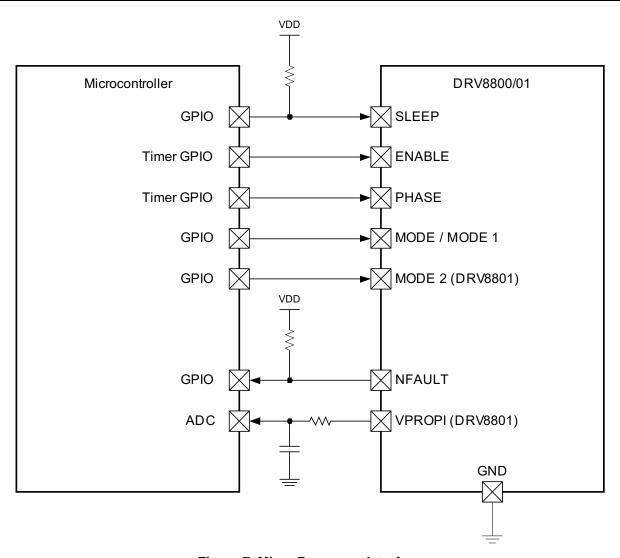


Figure 7. Micro Processor Interface

# 4.1 Pulse-Width Modulating ENABLE

The most common H-Bridge direction/speed control scheme is to use a conventional GPIO output for the PHASE (selects direction) and pulse-width modulate ENABLE for speed control.

#### 4.2 Pulse-Width Modulating PHASE

Another technique widely used is to use a speed/direction control scheme where ENABLE is connected to a GPIO output and the PHASE is pulse-width modulated. In this case, both direction and speed are controlled with a single signal. ENABLE is only used to disable the motor and stop all current flow.

When pulse-width modulating PHASE, a 50% duty cycle will stop the motor. Duty cycles above 50% will have the motor moving on the clockwise direction with proportional control; 100% duty cycle represents full speed.

Duty cycles below 50% will have the motor rotating with a counter clockwise direction; 0% duty cycle represents full speed.

#### **IMPORTANT NOTICE**

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

**Applications Products Amplifiers** amplifier.ti.com Audio www.ti.com/audio Data Converters Automotive www.ti.com/automotive dataconverter.ti.com DLP® Products Broadband www.dlp.com www.ti.com/broadband DSP Digital Control dsp.ti.com www.ti.com/digitalcontrol Clocks and Timers www.ti.com/clocks Medical www.ti.com/medical Military Interface www.ti.com/military interface.ti.com Optical Networking Logic logic.ti.com www.ti.com/opticalnetwork Power Mgmt power.ti.com Security www.ti.com/security Telephony Microcontrollers microcontroller.ti.com www.ti.com/telephony Video & Imaging www.ti-rfid.com www.ti.com/video RF/IF and ZigBee® Solutions www.ti.com/lprf Wireless www.ti.com/wireless

> Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2009, Texas Instruments Incorporated